

---

# TABLE OF CONTENTS

<b>Preface</b> .....	<b>xxi</b>
<b>Chapter One: Digital Signals and Systems</b> .....	<b>1</b>
1.1 Should Software Engineers Worry About Hardware?.....	1
1.2 Non-Digital Signals.....	3
1.3 Digital Signals.....	4
1.4 Conversion Systems.....	6
1.5 Representation of Digital Signals .....	7
1.6 Types of Digital Signals.....	9
1.6.1 Edges.....	9
1.6.2 Pulses.....	9
1.6.3 Non-Periodic Pulse Trains .....	10
1.6.4 Periodic Pulse Trains.....	11
1.6.5 Pulse-Width Modulation .....	13
1.7 Unit Prefixes .....	15
1.8 What's Next? .....	16
Problems.....	16
<b>Chapter Two: Numbering Systems</b> .....	<b>17</b>
2.1 Unsigned Binary Counting.....	17
2.2 Binary Terminology.....	20
2.3 Unsigned Binary to Decimal Conversion .....	20
2.4 Decimal to Unsigned Binary Conversion .....	23
2.5 Binary Representation of Analog Values.....	25
2.6 Sampling Theory.....	31
2.7 Hexadecimal Representation.....	34
2.8 Binary Coded Decimal.....	36
2.9 Gray Codes.....	37
2.10 What's Next? .....	40
Problems.....	41
<b>Chapter Three: Binary Math and Signed Representations</b> .....	<b>43</b>
3.1 Binary Addition.....	43
3.2 Binary Subtraction .....	45
3.3 Binary Complements.....	46
3.3.1 One's Complement .....	46
3.3.2 Two's Complement.....	47
3.3.3 Most Significant Bit as a Sign Indicator .....	50
3.3.4 Signed Magnitude .....	51

3.3.5 MSB and Number of Bits.....	51
3.3.6 Issues Surrounding the Conversion of Binary Numbers.....	52
3.3.7 Minimums and Maximums.....	55
3.4 Floating Point Binary.....	57
3.5 Hexadecimal Addition.....	61
3.6 BCD Addition.....	64
3.7 Multiplication and Division by Powers of Two.....	65
3.8 Easy Decimal to Binary Conversion Trick.....	67
3.9 Arithmetic Overflow.....	67
3.10 What's Next?.....	69
Problems.....	69
<b>Chapter Four: Logic Functions and Gates.....</b>	<b>71</b>
4.1 Logic Gate Basics.....	71
4.1.1 NOT Gate.....	72
4.1.2 AND Gate.....	72
4.1.3 OR Gate.....	73
4.1.4 Exclusive-OR (XOR) Gate.....	74
4.2 Truth Tables.....	75
4.3 Timing Diagrams for Gates.....	79
4.4 Combinational Logic.....	80
4.5 Truth Tables for Combinational Logic.....	83
4.6 What's Next?.....	86
Problems.....	87
<b>Chapter Five: Boolean Algebra.....</b>	<b>89</b>
5.1 Need for Boolean Expressions.....	89
5.2 Symbols of Boolean Algebra.....	90
5.3 Boolean Expressions of Combinational Logic.....	92
5.4 Laws of Boolean Algebra.....	95
5.5 Rules of Boolean Algebra.....	96
5.5.1 NOT Rule.....	96
5.5.2 OR Rules.....	96
5.5.3 AND Rules.....	97
5.5.4 XOR Rules.....	98
5.5.5 Derivation of Other Rules.....	99
5.6 Simplification.....	101
5.7 DeMorgan's Theorem.....	103
5.8 What's Next?.....	106
Problems.....	107

<b>Chapter Six: Standard Boolean Expression Formats.....</b>	<b>109</b>
6.1 Sum-of-Products .....	109
6.2 Converting an SOP Expression to a Truth Table.....	110
6.3 Converting a Truth Table to an SOP Expression.....	112
6.4 Product-of-Sums .....	114
6.5 Converting POS to Truth Table.....	115
6.6 Converting a Truth Table to a POS Expression.....	118
6.7 NAND-NAND Logic.....	119
6.8 What's Next? .....	122
Problems.....	123
<b>Chapter Seven: Karnaugh Maps .....</b>	<b>125</b>
7.1 The Karnaugh Map .....	125
7.2 Using Karnaugh Maps .....	129
7.3 "Don't Care" Conditions in a Karnaugh Map.....	137
7.4 What's Next? .....	138
Problems.....	139
<b>Chapter Eight: Combinational Logic Applications .....</b>	<b>141</b>
8.1 Adders .....	141
8.2 Seven-Segment Displays.....	147
8.3 Active-Low Signals.....	151
8.4 Decoders.....	152
8.5 Multiplexers .....	155
8.6 Demultiplexers.....	157
8.7 Integrated Circuits.....	159
8.8 What's Next? .....	163
Problems.....	164
<b>Chapter Nine: Binary Operation Applications .....</b>	<b>165</b>
9.1 Bitwise Operations.....	165
9.1.1 Clearing/Masking Bits .....	167
9.1.2 Setting Bits .....	171
9.1.3 Toggling Bits.....	171
9.2 Comparing Bits with XOR.....	173
9.3 Parity .....	174
9.4 Checksum.....	175
9.5 Cyclic Redundancy Check.....	179
9.5.1 CRC Process.....	185
9.5.2 CRC Implementation .....	187
9.6 Hamming Code .....	188

9.7 What's Next? .....	199
Problems .....	199
<b>Chapter Ten: Memory Cells .....</b>	<b>203</b>
10.1 New Truth Table Symbols .....	203
10.1.1 Edges/Transitions .....	203
10.1.2 Previously Stored Values .....	204
10.1.3 Undefined Values .....	204
10.2 The S-R Latch .....	205
10.3 The D Latch .....	209
10.4 Divide-By-Two Circuit .....	212
10.5 Counter .....	213
10.6 Parallel Data Output .....	214
10.7 What's Next? .....	215
Problems .....	216
<b>Chapter Eleven: State Machines .....</b>	<b>217</b>
11.1 Introduction to State Machines .....	217
11.1.1 States .....	217
11.1.2 State Diagrams .....	218
11.1.3 Errors in State Diagrams .....	222
11.1.4 Basic Circuit Organization .....	222
11.2 State Machine Design Process .....	225
11.3 Another State Machine Design: Pattern Detection .....	234
11.4 Mealy Versus Moore State Machines .....	237
11.5 What's Next? .....	238
Problems .....	239
<b>Chapter Twelve: Memory Organization .....</b>	<b>241</b>
12.1 Early Memory .....	241
12.2 Organization of Memory Device .....	242
12.3 Interfacing Memory to a Processor .....	244
12.3.1 Buses .....	244
12.3.2 Memory Maps .....	248
12.3.3 Address Decoding .....	250
12.3.4 Chip Select Hardware .....	255
12.4 Memory Mapped Input/Output .....	259
12.5 Memory Terminology .....	260
12.5.1 Random Access Memory .....	260
12.5.2 Read Only Memory .....	261
12.5.3 Static RAM versus Dynamic RAM .....	261

12.5.4 Types of DRAM and Their Timing .....	263
12.5.5 Asynchronous vs. Synchronous Memory .....	266
12.6 What's Next? .....	267
Problems.....	267
<b>Chapter Thirteen: Memory Hierarchy .....</b>	<b>269</b>
13.1 Characteristics of the Memory Hierarchy .....	269
13.2 Physical Characteristics of a Hard Drive .....	269
13.2.1 Hard Drive Read/Write Head.....	270
13.2.2 Data Encoding.....	272
13.2.3 Hard Drive Access Time .....	275
13.2.4 S.M.A.R.T. ....	278
13.3 Organization of Data on a Hard Drive .....	279
13.4 Cache RAM.....	284
13.4.1 Cache Organization.....	286
13.4.2 Dividing Memory into Blocks .....	287
13.4.3 Cache Operation.....	289
13.4.4 Cache Characteristics .....	290
13.4.5 Cache Mapping Functions.....	290
13.4.6 Cache Write Policy .....	299
13.5 Registers.....	300
13.6 What's Next? .....	300
Problems.....	301
<b>Chapter Fourteen: Serial Protocol Basics.....</b>	<b>303</b>
14.1 OSI Seven-Layer Network Model .....	303
14.2 Serial versus Parallel Data Transmission.....	304
14.3 Anatomy of a Frame or Packet .....	306
14.4 Sample Protocol: IEEE 802.3 Ethernet.....	308
14.5 Sample Protocol: Internet Protocol.....	310
14.6 Sample Protocol: Transmission Control Protocol.....	313
14.7 Dissecting a Frame.....	317
14.8 Additional Resources .....	320
14.9 What's Next? .....	322
Problems.....	322
<b>Chapter Fifteen: Introduction to Processor Architecture.....</b>	<b>325</b>
15.1 Organization versus Architecture.....	325
15.2 Components .....	325
15.2.1 Bus.....	325
15.2.2 Registers.....	326

15.2.3	Flags	327
15.2.4	Buffers	328
15.2.5	The Stack	329
15.2.6	I/O Ports	331
15.3	Processor Level	332
15.4	CPU Level	333
15.5	Simple Example of CPU Operation	334
15.6	Assembly and Machine Language	338
15.7	Big-Endian/Little-Endian	345
15.8	Pipelined Architectures	346
15.9	Passing Data To and From Peripherals	350
15.9.1	Memory-Mapped I/O	351
15.9.2	Polling	353
15.9.3	Interrupts	354
15.9.4	Direct Memory Access	355
15.9.5	I/O Channels and Processors	356
15.10	What's Next?	357
	Problems	357
<b>Chapter Sixteen: Intel 80x86 Base Architecture</b>		<b>359</b>
16.1	Why Study the 80x86?	359
16.2	Execution Unit	360
16.2.1	General Purpose Registers	361
16.2.2	Address Registers	362
16.2.3	Flags	363
16.2.4	Internal Buses	365
16.3	Bus Interface Unit	365
16.3.1	Segment Addressing	366
16.3.2	Instruction Queue	370
16.4	Memory versus I/O Ports	371
16.5	What's Next?	372
	Problems	373
<b>Chapter Seventeen: Intel 80x86 Assembly Language</b>		<b>375</b>
17.1	Assemblers versus Compilers	375
17.2	Components of a Line of Assembly Language	376
17.3	Assembly Language Directives	378
17.3.1	SEGMENT Directive	378
17.3.2	.MODEL, .STACK, .DATA, and .CODE Directives	380
17.3.3	PROC Directive	381

- 17.3.4 END Directive..... 382
- 17.3.5 Data Definition Directives ..... 382
- 17.3.6 EQU Directive..... 383
- 17.4 80x86 Opcodes..... 385
  - 17.4.1 Data Transfer..... 385
  - 17.4.2 Data Manipulation..... 386
  - 17.4.3 Program Control..... 387
  - 17.4.4 Special Operations ..... 390
- 17.5 Addressing Modes..... 391
  - 17.5.1 Register Addressing ..... 391
  - 17.5.2 Immediate Addressing..... 392
  - 17.5.3 Pointer Addressing..... 392
- 17.6 Sample 80x86 Assembly Language Programs..... 393
- 17.7 Additional 80x86 Programming Resources ..... 397
- 17.8 What's Next? ..... 398
- Problems..... 398

**Index ..... 401**

**TABLE OF FIGURES**

- 1-1 Sample Digital System..... 3
- 1-2 Continuous Analog Signal with Infinite Resolution ..... 4
- 1-3 Sample of Discrete Measurements Taken Every 0.1 Sec..... 4
- 1-4 Samples Taken of an Analog Signal ..... 5
- 1-5 Slow Sampling Rate Missed an Anomaly..... 5
- 1-6 Poor Resolution Resulting in an Inaccurate Measurement ..... 5
- 1-7 Block Diagram of a System to Capture Analog Data ..... 6
- 1-8 Representation of a Single Binary Signal ..... 8
- 1-9 Representation of Multiple Digital Signals..... 8
- 1-10 Alternate Representation of Multiple Digital Signals..... 9
- 1-11 Digital Transition Definitions ..... 10
- 1-12 Pulse Waveforms ..... 10
- 1-13 Non-Periodic Pulse Train..... 10
- 1-14 Periodic Pulse Train ..... 11
- 1-15 Periodic Pulse Train with Different Pulse Widths ..... 11
- 1-16 Periodic Pulse Train with 25% Duty Cycle ..... 13
- 2-1 Counting in Decimal ..... 17

2-2	Counting in Binary.....	18
2-3	Binary-Decimal Equivalents from 0 to 17.....	19
2-4	Values Represented By Each of the First 8 Bit Positions.....	21
2-5	Sample Conversion of $10110100_2$ to Decimal.....	21
2-6	Decimal to Unsigned Binary Conversion Flow Chart.....	24
2-7	Sample Analog Signal of Sound.....	26
2-8	Effects of Number of Bits on Roundoff Error.....	32
2-9	Aliasing Effects Due to Slow Sampling Rate.....	33
2-10	Eight Binary Values Identifying Rotating Shaft Position.....	38
2-11	Example of a Position Encoder.....	38
2-12	Conversion from Unsigned Binary to Gray Code.....	39
3-1	Four Possible Results of Adding Two Bits.....	44
3-2	Four Possible Results of Adding Two Bits with Carry.....	44
3-3	Two's Complement Short-Cut.....	49
3-4	Converting a Two's Complement Number to a Decimal.....	53
3-5	IEEE Standard 754 Floating-Point Formats.....	59
3-6	Duplicate MSB for Right Shift of 2's Complement Values.....	66
4-1	Basic Format of a Logic Gate.....	71
4-2	Basic Logic Symbols.....	72
4-3	Operation of the NOT Gate.....	72
4-4	Operation of a Two-Input AND Gate.....	73
4-5	Operation of a Two-Input OR Gate.....	74
4-6	Operation of a Two-Input XOR Gate.....	74
4-7	Sample Three-Input Truth Table.....	75
4-8	Listing All Bit Patterns for a Four-Input Truth Table.....	76
4-9	Inverter Truth Table.....	77
4-10	Two-Input AND Gate Truth Table.....	77
4-11	Two-Input OR Gate Truth Table.....	77
4-12	Two-Input XOR Gate Truth Table.....	78
4-13	Three-Input AND Gate Truth Table With Don't Cares.....	78
4-14	Sample Timing Diagram for a Three-Input AND Gate.....	79
4-15	Sample Timing Diagram for a Three-Input OR Gate.....	79
4-16	Sample Timing Diagram for a Three-Input XOR Gate.....	79
4-17	Sample Combinational Logic.....	80
4-18	Combinational Logic for a Simple Security System.....	80
4-19	Truth Table for Simple Security System of Figure 4-18.....	81
4-20	"NOT" Circuits.....	82
4-21	Schematic "Short-Hand" for Inverted Inputs.....	82



4-22	Sample of Multi-Level Combinational Logic .....	83
4-23	Process of Passing Inputs Through Combinational Logic .....	83
4-24	Steps That Inputs Pass Through in Combinational Logic.....	84
4-25	All Combinations of Ones and Zeros for Three Inputs.....	84
4-26	Step (a) in Sample Truth Table Creation .....	85
4-27	Step (b) in Sample Truth Table Creation .....	85
4-28	Step (c) in Sample Truth Table Creation .....	86
4-29	Step (d) in Sample Truth Table Creation .....	86
5-1	Schematic and Truth Table of Combinational Logic .....	89
5-2	Boolean Expression for the AND Function .....	90
5-3	Boolean Expression for the OR Function .....	91
5-4	Boolean Expression for the NOT Function.....	91
5-5	Circuit Representation of the Boolean Expression $1+0+1$ .....	91
5-6	Sample of Multi-Level Combinational Logic .....	92
5-7	Creating Boolean Expression from Combinational Logic .....	93
5-8	Examples of the Precedence of the NOT Function .....	93
5-9	Example of a Conversion from a Boolean Expression .....	94
5-10	Commutative Law for Two Variables OR'ed Together .....	95
5-11	Schematic Form of NOT Rule .....	96
5-12	Rules of Boolean Algebra .....	101
5-13	Application of DeMorgan's Theorem.....	105
5-14	Schematic Application of DeMorgan's Theorem.....	106
6-1	Sample Sum-of-Products Binary Circuit .....	110
6-2	Samples of Single Product (AND) Truth Tables .....	111
6-3	Sample of a Sum-of-Products Truth Table .....	111
6-4	Conversion of an SOP Expression to a Truth Table .....	112
6-5	Sample Product-of-Sums Binary Circuit .....	115
6-6	Samples of Single Sum (OR) Truth Tables.....	115
6-7	Sample of a Product-of-Sums Truth Table .....	116
6-8	Sample Sums With Multiple Zero Outputs.....	117
6-9	Conversion of a POS Expression to a Truth Table .....	118
6-10	Circuit Depiction of DeMorgan's Theorem.....	120
6-11	OR Gate Equals a NAND Gate With Inverted Inputs.....	120
6-12	OR-to-NAND Equivalency Expanded to Four Inputs .....	120
6-13	Sample SOP Circuit .....	121
6-14	Sample SOP Circuit with Output OR Gate Replaced .....	121
6-15	Sample SOP Circuit Implemented With NAND Gates.....	122
7-1	2-by-2 Karnaugh Map Used with Two Inputs .....	126

7-2	Mapping a 2-Input Truth Table to Its Karnaugh Map .....	126
7-3	Three-Input Karnaugh Map .....	127
7-4	Four-Input Karnaugh Map .....	127
7-5	Identifying the Products in a Karnaugh Map .....	130
7-6	Karnaugh Map with Four Adjacent Cells Containing '1' .....	130
7-7	Sample Rectangle in a Three-Input Karnaugh Map.....	133
7-8	Karnaugh Map with a "Don't Care" Elements .....	138
7-9	Karnaugh Map with a "Don't Care" Elements Assigned .....	138
8-1	Four Possible Results of Adding Two Bits.....	141
8-2	Block Diagram of a Half Adder.....	142
8-3	Four Possible States of a Half Adder .....	142
8-4	Logic Circuit for a Half Adder.....	143
8-5	Block Diagram of a Multi-bit Adder.....	144
8-6	Block Diagram of a Full Adder.....	144
8-7	Sum and Carryout Karnaugh Maps for a Full Adder.....	145
8-8	Logic Circuit for a Full Adder .....	146
8-9	Seven-Segment Display .....	147
8-10	Displaying a '1' with a 7-Segment Display .....	147
8-11	A Seven-Segment Display Displaying a Decimal '2' .....	148
8-12	Block Diagram of a Seven-Segment Display Driver.....	148
8-13	Segment Patterns for all Hexadecimal Digits .....	149
8-14	Seven Segment Display Truth Table .....	149
8-15	Karnaugh Map for Segment 'e'.....	150
8-16	Karnaugh Map for Segment 'e' with Rectangles.....	150
8-17	Logic Circuit for Segment e of 7-Segment Display.....	151
8-18	Labeling Conventions for Active-Low Signals .....	152
8-19	Sample Circuit for Enabling a Microwave .....	153
8-20	Sample Circuit for Delivering a Soda.....	153
8-21	Truth Table to Enable a Device for A=1, B=1, & C=0.....	154
8-22	Digital Circuit for a 1-of-4 Decoder .....	154
8-23	Digital Circuit for an Active-Low 1-of-4 Decoder .....	155
8-24	Truth Table for an Active-Low 1-of-8 Decoder .....	155
8-25	Block Diagram of an Eight Channel Multiplexer .....	156
8-26	Truth Table for an Eight Channel Multiplexer .....	156
8-27	Logic Circuit for a 1-Line-to-4-Line Demultiplexer.....	158
8-28	Truth Table for a 1-Line-to-4-Line Demultiplexer.....	159
8-29	Examples of Integrated Circuits.....	159
8-30	Pin-out of a Quad Dual-Input NAND Gate IC (7400).....	160
8-31	Sample Pin 1 Identifications .....	160

8-32	Generic Protoboard .....	161
8-33	Generic Protoboard Internal Connections .....	161
8-34	Sample Circuit Wired on a Protoboard .....	162
8-35	Schematic Symbol of a Light-Emitting Diode (LED) .....	162
8-36	LED Circuit .....	163
8-37	Switch Circuit.....	163
9-1	Graphic of a Bitwise Operation Performed on LSB .....	166
9-2	Bitwise AND of $01101011_2$ and $11011010_2$ .....	166
9-3	Three Sample Bitwise ANDs .....	168
9-4	Possible Output from a Motion Detector .....	173
9-5	A Difference in Output Indicates an Error .....	173
9-6	Simple Error Detection with an XOR Gate.....	174
9-7	Sample Block of Data with Accompanying Datasums .....	176
9-8	Small Changes in Data Canceling in Checksum.....	179
9-9	Example of Long Division in Binary .....	181
9-10	Example of Long Division Using XOR Subtraction.....	182
9-11	Sample Code for Calculating CRC Checksums.....	189
9-12	Venn Diagram Representation of Hamming Code .....	192
9-13	Example Single-Bit Errors in Venn Diagram .....	192
9-14	Example of a Two-Bit Error .....	193
9-15	Using Parity to Check for Double-Bit Errors.....	194
10-1	Symbols for Rising Edge and Falling Edge Transitions .....	204
10-2	Sample Truth Table Using Undefined Output .....	204
10-3	Primitive Feedback Circuit using Inverters.....	205
10-4	Operation of a NAND Gate with One Input Tied High .....	206
10-5	Primitive Feedback Circuit Redrawn with NAND Gates .....	206
10-6	Only Two Possible States of Circuit in Figure 10-5 .....	206
10-7	Operation of a Simple Memory Cell .....	207
10-8	Operation of a Simple Memory Cell (continued).....	208
10-9	S-R Latch .....	209
10-10	S-R Latch Truth Table .....	209
10-11	Block Diagram of the D Latch .....	209
10-12	Edge-Triggered D Latch Truth Tables .....	211
10-13	Transparent D Latch Truth Tables .....	211
10-14	Divide-By-Two Circuit .....	212
10-15	Clock and Output Timing in a Divide-By-Two Circuit .....	212
10-16	Cascading Four Divide-By-Two Circuits .....	213
10-17	Counter Implemented with Divide-By-Two Circuits .....	213

10-18	Output of Binary Counter Circuit .....	214
10-19	Output Port Data Latch Circuitry.....	215
11-1	Adding Memory to a Digital Logic Circuit .....	217
11-2	States of a Traffic Signal System.....	218
11-3	States of a Light Bulb.....	218
11-4	State Diagram for Light Bulb State Machine.....	218
11-5	Complete State Diagram for Light Bulb State Machine .....	219
11-6	Block Diagram of an Up-Down Binary Counter .....	220
11-7	State Diagram for a 3-Bit Up-Down Binary Counter .....	221
11-8	Sample of a Reset Indication in a State Diagram.....	221
11-9	Block Diagram of a State Machine .....	223
11-10	Initial State of the Push Button Light Control .....	226
11-11	Transitions from State 0 of Push Button Circuit.....	226
11-12	B=0 Transition from State 0 of Push Button Circuit .....	227
11-13	B=1 Transition from State 0 of Push Button Circuit .....	227
11-14	B=0 Transition from State 1 of Push Button Circuit .....	227
11-15	B=1 Transition from State 1 of Push Button Circuit .....	228
11-16	Transitions from State 2 of Push Button Circuit.....	228
11-17	Final State Diagram for Push Button Circuit.....	229
11-18	Block Diagram for Push Button Circuit.....	230
11-19	K-Maps for $S_1'$ , $S_0'$ , and L of Push Button Circuit.....	232
11-20	Finished Push Button Circuit .....	232
11-21	Revised Truth Table and K Map for Push Button Circuit .....	233
11-22	Identifying the Bit Pattern "101" in a Bit Stream .....	234
11-23	State Diagram for Identifying the Bit Pattern "101" .....	235
11-24	Next State and Output Truth Tables for Pattern Detect.....	236
11-25	K-Maps for $S_1'$ , $S_0'$ , and P of Pattern Detect Circuit .....	237
11-26	Final Circuit to Identify the Bit Pattern "101" .....	237
11-27	Basic Configuration of a Mealy Machine .....	238
11-28	Sample State Diagram of a Mealy Machine .....	238
11-29	Output Truth Table for Sample Mealy Machine.....	239
12-1	Diagram of a Section of Core Memory.....	241
12-2	Basic Organization of a Memory Device.....	243
12-3	Basic Processor to Memory Device Interface.....	245
12-4	Two Memory Devices Sharing a Bus .....	246
12-5	Three Buffers Trying to Drive the Same Output .....	248
12-6	Sample Memory Maps .....	249
12-7	Full Address with Enable Bits and Device Address Bits.....	251

12-8	IPv4 Address Divided into Subnet and Host IDs.....	254
12-9	Sample Chip Select Circuit for a Memory Device.....	256
12-10	Some Types of Memory Mapped I/O Configurations .....	260
12-11	Basic Addressing Process for a DRAM.....	264
12-12	Organization of DRAM.....	265
12-13	Example of an FPM Transfer.....	265
12-14	Example of an EDO Transfer.....	266
13-1	Block Diagram of a Standard Memory Hierarchy .....	269
13-2	Configuration of a Hard Drive Write Head.....	271
13-3	Sample FM Magnetic Encoding.....	273
13-4	Sample MFM Magnetic Encoding.....	274
13-5	RLL Relation between Bit Patterns and Polarity Changes ...	274
13-6	Sample RLL Magnetic Encoding.....	275
13-7	Components of Disk Access Time.....	277
13-8	Relation between Read/Write Head and Tracks .....	279
13-9	Organization of Hard Disk Platter.....	280
13-10	Illustration of a Hard Drive Cylinder .....	281
13-11	Equal Number of Bits per Track versus Equal Sized Bits .....	282
13-12	Comparison of Sector Organizations .....	282
13-13	Cache Placement between Main Memory and Processor .....	285
13-14	L1 and L2 Cache Placement.....	285
13-15	Split Cache Organization .....	286
13-16	Organization of Cache into Lines .....	287
13-17	Division of Memory into Blocks.....	288
13-18	Organization of Address Identifying Block and Offset .....	289
13-19	Direct Mapping of Main Memory to Cache.....	291
13-20	Direct Mapping Partitioning of Memory Address .....	292
13-21	Fully Associative Partitioning of Memory Address.....	295
13-22	Set Associative Mapping of Main Memory to Cache .....	297
13-23	Effect of Cache Set Size on Address Partitioning.....	298
14-1	Sample Protocol Stack using TCP, IP, and Ethernet .....	307
14-2	Layout of an IEEE 802.3 Ethernet Frame .....	308
14-3	Layout of an IP Packet Header.....	311
14-4	Layout of a TCP Packet Header.....	314
14-5	Position and Purpose of TCP Control Flags .....	315
14-6	Layout of a TCP Pseudo Header.....	316
14-7	Simulated Raw Data Capture of an Ethernet Frame .....	317
15-1	Sample Code Using Conditional Statements .....	328

15-2	Block Diagram of a System Incorporating a Buffer .....	329
15-3	Generic Block Diagram of a Processor System .....	332
15-4	Generic Block Diagram of Processor Internals.....	333
15-5	Generic Block Diagram of a Typical CPU .....	334
15-6	Decoded Assembly Language from Table 15-6 .....	343
15-7	Non-Pipelined Execution of Five Instructions.....	348
15-8	Pipelined Execution of Five Instructions .....	348
15-9	Sample Memory Mapped Device Circuit .....	352
15-10	Basic Operation of an ISR .....	355
16-1	Block Diagram of 80x86 Execution Unit (EU) .....	360
16-2	Block Diagram of 80x86 Bus Interface Unit (BIU).....	366
16-3	Segment/Pointer Relation in the 80x86 Memory Map .....	368
17-1	Format of a Line of Assembly Language Code .....	377
17-2	Format and Parameters Used to Define a Segment.....	379
17-3	Format of the .MODEL Directive.....	380
17-4	Format and Parameters Used to Define a Procedure .....	381
17-5	Format and Parameters of Some Define Directives.....	383
17-6	Example Uses of Define Directives .....	384
17-7	Format and Parameters of the EQU Directive .....	384
17-8	Sample Code with and without the EQU Directive .....	384
17-9	Format and Parameters of the MOV Opcode.....	385
17-10	Format and Parameters of the IN and OUT Opcodes .....	385
17-11	Format and Parameters of the ADD Opcode .....	386
17-12	Format and Parameters of NEG, NOT, DEC, and INC .....	386
17-13	Format and Parameters of SAR, SHR, SAL, and SHL.....	387
17-14	Example of a JMP Instruction.....	387
17-15	Example of a LOOP Instruction.....	389
17-16	Sample Organization of a Procedure Call.....	390
17-17	Examples of Register Addressing .....	392
17-18	Examples of Immediate Addressing .....	392
17-19	Examples of an Address being used as an Operand.....	393
17-20	Skeleton Code for a Simple Assembly Program.....	393
17-21	Code to Assign Data Segment Address to DS Register.....	394
17-22	Code to Inform O/S that Program is Terminated.....	395
17-23	Skeleton Code with Code Added for O/S Support .....	395
17-24	Data Defining Directives for Example Code .....	396
17-25	Step-by-Step Example Operation Converted to Code .....	396
17-26	Final Code for Example Assembly Language Program.....	397

---

**TABLE OF TABLES**

1-1	Unit Prefixes.....	15
2-1	Converting Binary to Decimal and Hexadecimal .....	35
2-2	Converting BCD to Decimal.....	36
2-3	Derivation of the Four-Bit Gray Code .....	40
3-1	Representation Comparison for 8-bit Binary Numbers .....	57
3-2	Hexadecimal to Decimal Conversion Table.....	62
3-3	Multiplying the Binary Value $1001_2$ by Powers of Two.....	65
8-1	Addition Results Based on Inputs of a Full Adder .....	144
8-2	Sum and Carryout Truth Tables for a Full Adder .....	145
9-1	Truth Table for a Two-Input XOR Gate .....	172
9-2	Addition and Subtraction Without Carries or Borrows.....	181
9-3	Reconstructing the Dividend Using XORs .....	183
9-4	Second Example of Reconstructing the Dividend.....	184
9-5	Data Groupings and Parity for the Nibble $1011_2$ .....	190
9-6	Data Groupings with a Data Bit in Error .....	190
9-7	Data Groupings with a Parity Bit in Error .....	191
9-8	Identifying Errors in a Nibble with Three Parity Bits.....	191
9-9	Parity Bits Required for a Specific Number of Data Bits .....	195
9-10	Membership of Data and Parity Bits in Parity Groups .....	197
11-1	List of States for Push Button Circuit .....	230
11-2	Next State Truth Table for Push Button Circuit.....	231
11-3	Output Truth Table for Push Button Circuit .....	231
11-4	Revised List of States for Push Button Circuit .....	233
11-5	List of States for Bit Pattern Detection Circuit .....	236
12-1	The Allowable Settings of Four Chip Selects .....	247
12-2	Sample Memory Sizes versus Required Address Lines.....	251
15-1	Conditional Jumps to be Placed After a Compare .....	337
15-2	Conditional Jumps to be Placed After an Operation .....	338
15-3	Numbered Instructions for Imaginary Processor .....	340
15-4	Assembly Language for Imaginary Processor .....	340
15-5	Operand Requirements for Imaginary Processor .....	341
15-6	A Simple Program Stored at Memory Address $1000_{16}$ .....	342
15-7	Signal Values for Sample I/O Device .....	351
15-8	Control Signal Levels for I/O and Memory Transactions.....	353

16-1	Summary of Intel 80x86 Bus Characteristics .....	360
16-2	Summary of the 80x86 Read and Write Control Signals.....	372
17-1	Memory Models Available for use with .MODEL .....	381
17-2	Summary of 80x86 Conditional Jumps.....	388
17-3	80x86 Instructions for Modifying Flags .....	390